

# Single Clock Domain Designs

## Reset and Initialization

## Modelling FSMs in VHDL

---

LECTURE 4

IOULIIA SKLIAROVA

# Single Clock Domain Designs

---

A **clock domain** is the subset of the system components that are synchronized by a single clock signal.


Utilization of two or more clock domains in a system is frequently required but can lead to complex timing issues.

**Recommendation:** in all your projects you should:

- Use only the “clk” clock signal, or other clock derived from it (using a clock frequency divider or a clock IP).
- Use a single clock signal in conjunction with enable pulses to synchronize/sequence slower operations.
- All the components are synchronized by the same clock signal and each one has its own enable(s).



# Single Clock Domain with Enables

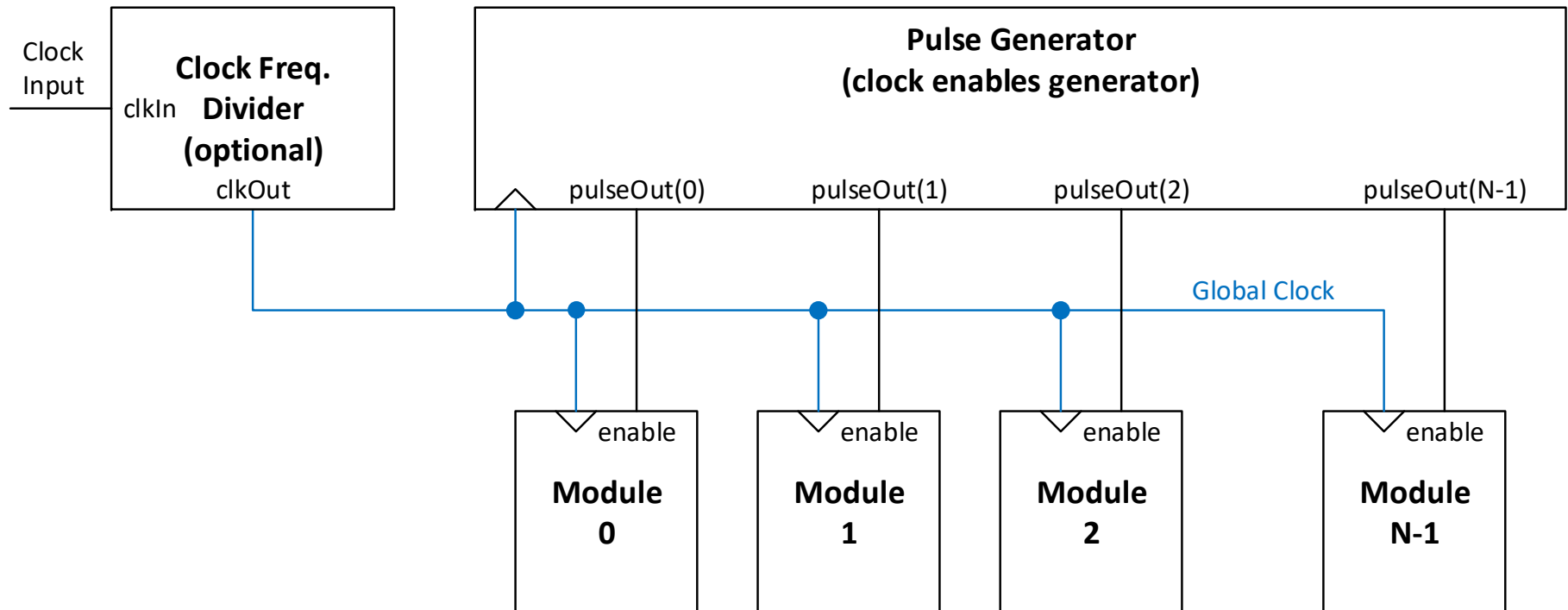

# Example of a Pulse Generator

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity pulse_gen is
    Port ( clk : in STD_LOGIC;
          reset : in STD_LOGIC;
          pulse : out STD_LOGIC);
end pulse_gen;

architecture Behavioral of pulse_gen is
    constant MAX : natural := 100_000_000;
    signal s_cnt : natural range 0 to MAX-1;
begin

    process(clk)
    begin
        if (rising_edge(clk)) then
            pulse <= '0';
            if (reset = '1') then
                s_cnt <= 0;
            else
                s_cnt <= s_cnt + 1;
                if (s_cnt = MAX-1) then
                    s_cnt <= 0;
                    pulse <= '1';
                end if;
            end if;
        end if;
    end process;

end Behavioral;
```



What is the active duration the output pulse?

What is the frequency of pulse output?

# Example of a Pulse Generator

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity generator is
    generic (NUMBER_STEPS : positive := 50_000_000);
    Port ( clk      : in STD_LOGIC;
          reset    : in STD_LOGIC;
          blink    : out STD_LOGIC);
end generator;

architecture Behavioral of generator is
    signal s_counter : natural range 0 to NUMBER_STEPS-1;
begin

    count_proc: process (clk)
    begin
        if rising_edge(clk) then
            if (reset = '1') or (s_counter >= NUMBER_STEPS-1) then
                s_counter <= 0;
            else
                s_counter <= s_counter + 1;
            end if;
            blink <= '1' when s_counter >= (NUMBER_STEPS/2) else '0'; -- VHDL-2008 !
        end if;
    end process;

end Behavioral;
```



What is the duty-cycle of the output blink?

What is the frequency of blink output?


# Initialization and Reset

Most sequential circuits require the initialization of their memory elements (e.g. FSM state register, counters, accumulators, etc.)


The initialization must be performed

- at system boot / after FPGA programming
- whenever needed, through the activation of global or local reset signals

 
Use of asynchronous reset can easily create circuits that glitch => synchronous reset components must be preferred



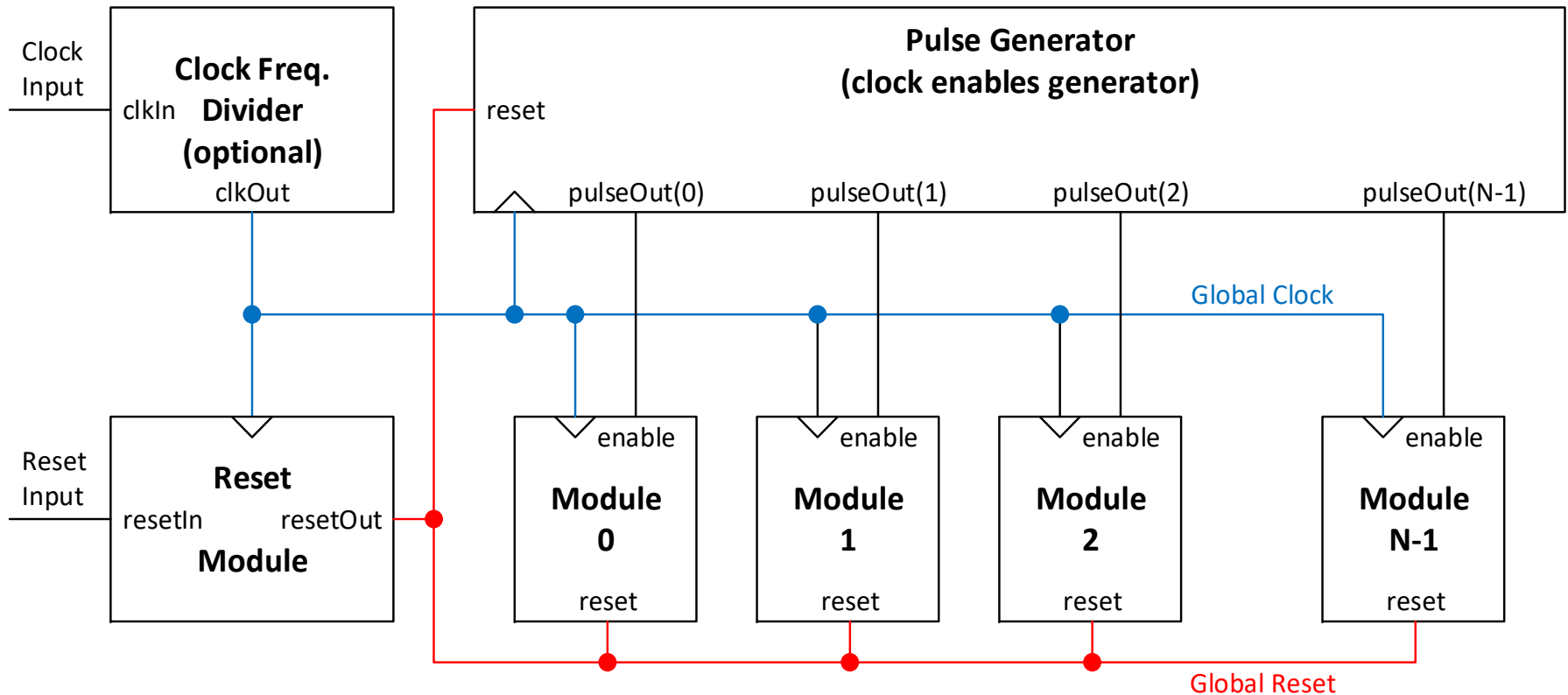
# Single Clock Domain with Enables and Reset



# Example of the Reset Module

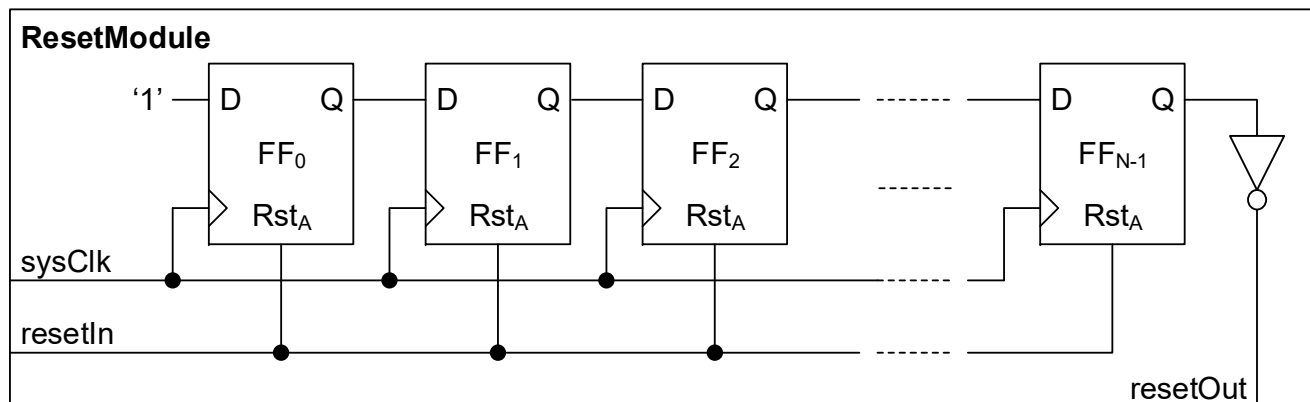

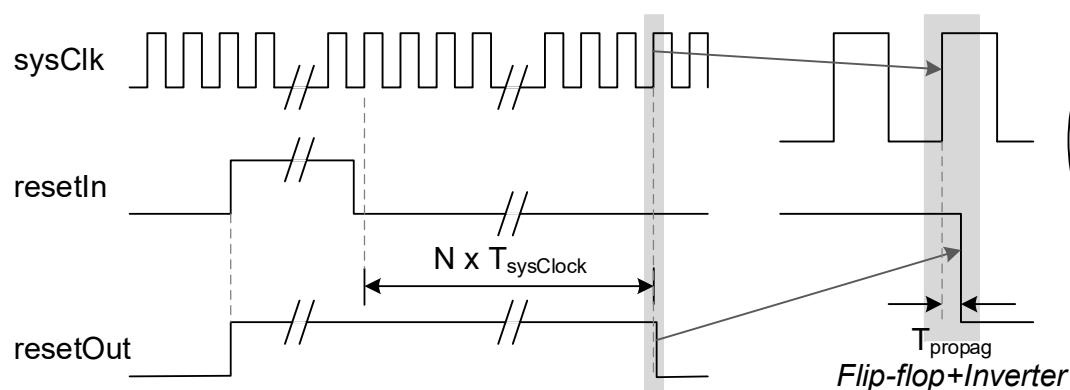After FPGA programming, all the FFs are loaded with 0's and the module activates the reset output



Circuit (synchron. with "sysClk") that uses the reset signal

All the system components must use preferably synchronous resets

The clock period and the number of flip-flops ensure a minimum reset activation time



# Example of the Reset Module

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity ResetModule is
    generic(N : positive := 4);
    port(sysClk : in std_logic;
         resetIn : in std_logic;
         resetOut : out std_logic);
end ResetModule;

architecture Behavioral of ResetModule is
    signal s_shiftReg : std_logic_vector((N - 1) downto 0) := (others => '0');
begin
    assert(N >= 2);


    shift_proc : process(resetIn, sysClk)
    begin
        if (resetIn = '1') then
            s_shiftReg <= (others => '0');
        elsif (rising_edge(sysClk)) then
            s_shiftReg((N - 1) downto 1) <= s_shiftReg((N - 2) downto 0);
            s_shiftReg(0) <= '1';
        end if;
    end process;

    resetOut <= not s_shiftReg(N - 1);
end Behavioral;


```

Generates a reset pulse, with the duration  
 $\sim N \times \text{sysClk}$  periods

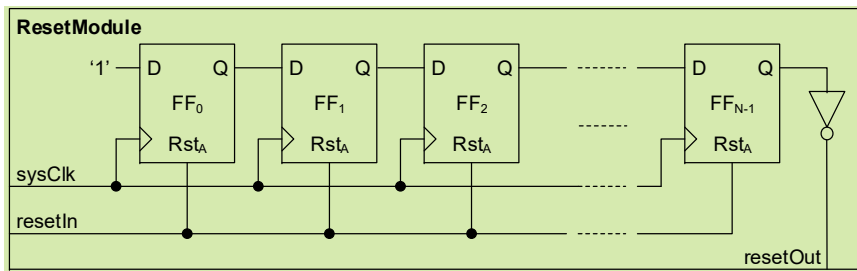Initialization of the **s\_shiftReg**  
 signal during FPGA programming



# Input Debouncing

 


E-learning:

```
entity DebounceUnit is
    generic (kHzClkFreq      : positive := 50000;
            mSecMinInWidth  : positive := 100;
            inPolarity       : std_logic := '0';
            outPolarity      : std_logic := '1');
    port (refClk      : in  std_logic;
          dirtyIn     : in  std_logic;
          pulsedOut   : out std_logic);
end DebounceUnit;
```

debounce\_BTNC:
 
```
entity work.DebounceUnit (Behavioral)
    generic map (kHzClkFreq => 100_000,
                mSecMinInWidth => 100,
                inPolarity => '1',
                outPolarity => '1')
    port map (refClk => clk,
              dirtyIn => btnC,
              pulsedOut => s_startStop);
```




# Computational System

## Datapath (execution unit)

- Components
  - Functional
  - Routing
  - Storage

## Controlpath

- Control unit
  - FSM(s)

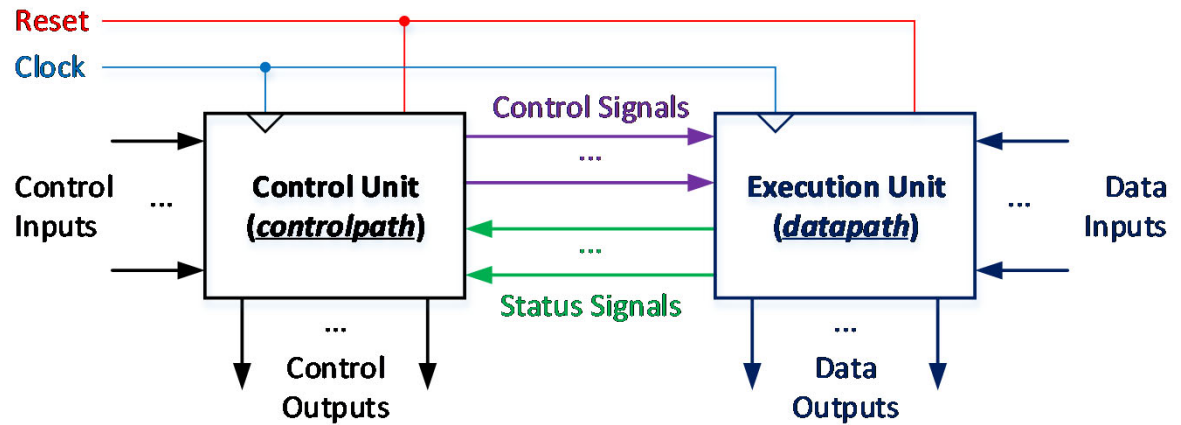


## *Controlpath - datapath interconnection*


- Control signals (controlpath → datapath)
- Status signals (controlpath ← datapath)

# FSM Structure

Moore:

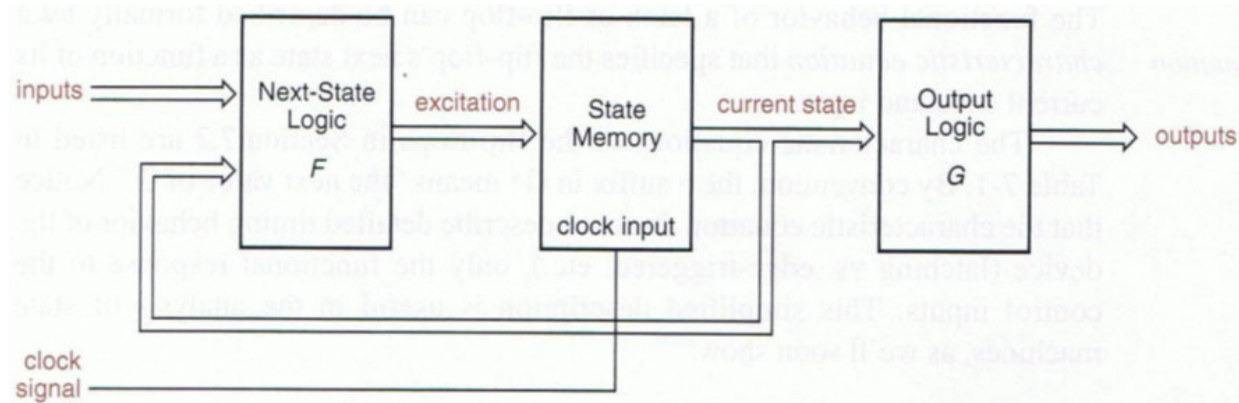


Mealy:

 
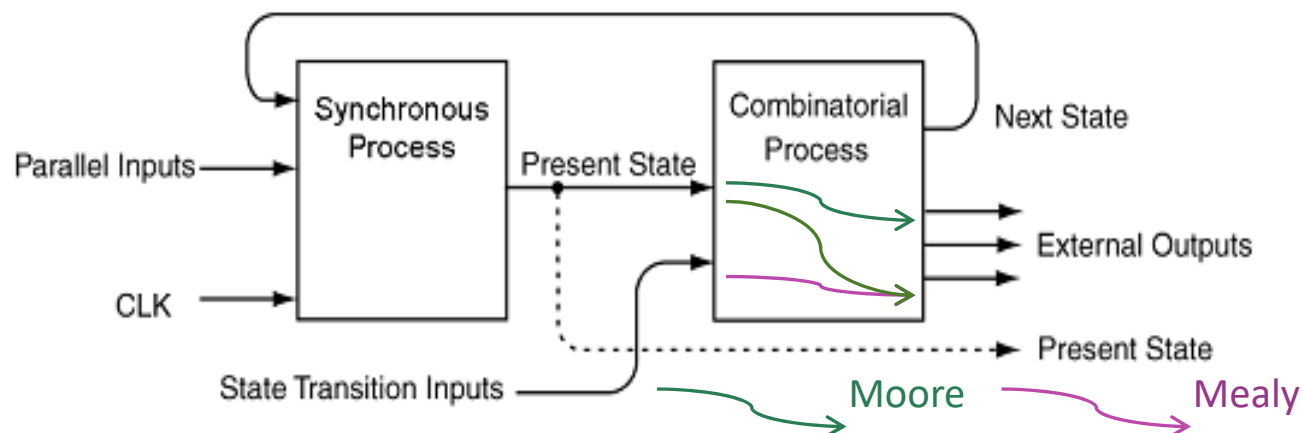
# Modelling FSMs in VHDL

Two VHDL processes:

- State memory (synchronous process)
- Combinational circuit (next state logic + output logic)
  - Depending on the way outputs are assigned
    - *Moore* (outputs depend only on the current state)
    - *Mealy* (outputs depend on both the current state and FSM inputs)
  - Ensure a value is always assigned to next state and outputs
    - Must be a combinational circuit – no latches!!!



# VHDL Coding

---

VHDL coding:

- There exist many different styles.
- The style explained here considers two processes: one for the state transitions, and another for the outputs.

Required steps:

- Have your state-transition diagram ready.
- The coding then just simply follows the state diagram.
- We need to define a custom user data type (e.g., “state”) to represent the states:

```
type state is (STOPPED, STARTED, BUSY);
```

```
signal y: state;
```


Two processes must be constructed:

- Sync\_proc: it is where the state transitions (that occur on the clock edge) are described.
- Comb\_proc: this is a combinational circuit where next state and outputs are defined based on the current state (and input signals).
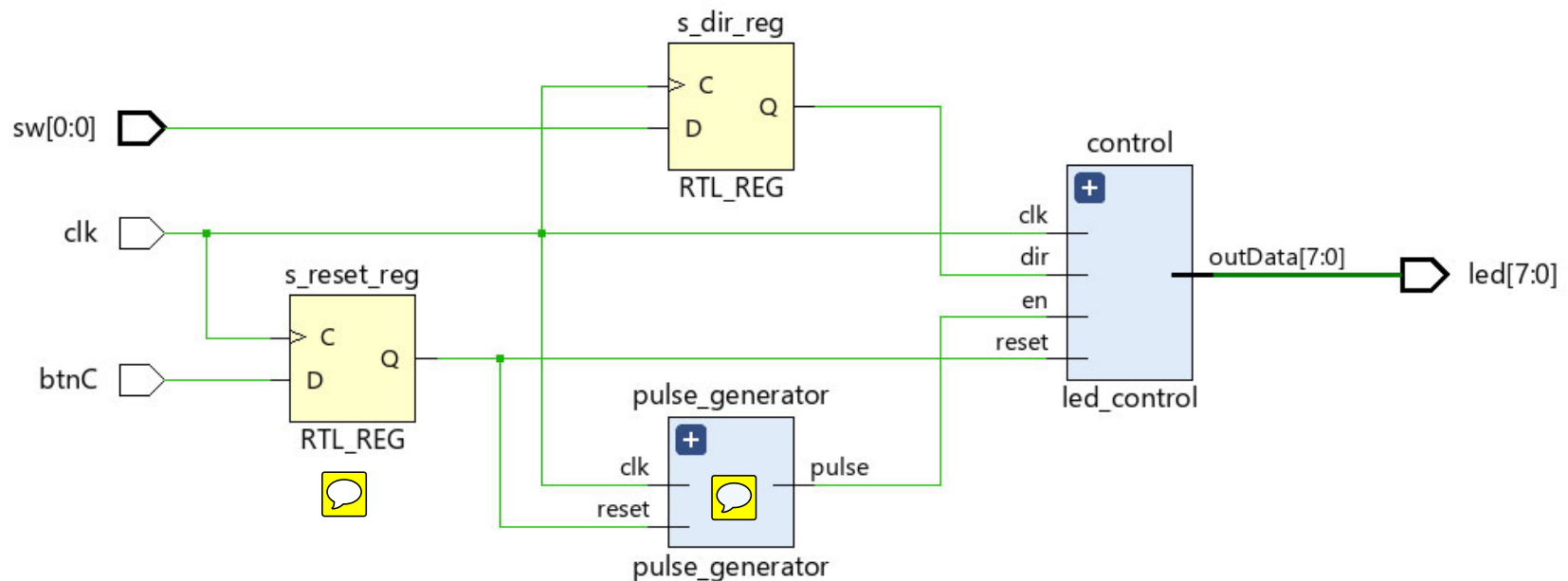
# Example: LED Sequence Controller


Sequence: 00000011, 00001111, 00111111, 11111100 when sw(0) = '0',  
or 11000000, 11110000, 11111100, 00111111 when sw(0) = '1'

The FSM includes an enable that allows for state transitions with frequency of 2Hz.


 
# State Diagram

Sequence: 00000011, 00001111, 00111111, 11111100 when sw(0) = '0',  
or 11000000, 11110000, 11111100, 00111111 when sw(0) = '1'





# Specification in VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity led_control is
    port (clk      : in  std_logic;
          en       : in  std_logic;
          reset    : in  std_logic;
          dir      : in  std_logic;
          outData  : out std_logic_vector(7 downto 0));
end led_control;

architecture Behavioral of led_control is
    type TState is (CLEAR, S1, S2, S3, S4);
    signal pState, nState: TState;

    signal s_data : std_logic_vector(outData'range) :=
        (others => '0');

begin
    sync_proc : process (clk)
    begin
        if (rising_edge(clk)) then
            if (reset = '1') then
                pState <= CLEAR;
            elsif en = '1' then
                pState <= nState;
            end if;
        end if;
    end process;

```

 

```

    comb_proc : process (pState, dir)
    begin
        case pState is
            when CLEAR =>
                s_data <= (others => '0');
                nState <= S1;
            when S1 =>
                if dir = '0' then --left
                    s_data <= "00000011";
                else
                    s_data <= "11000000";
                end if;
                nState <= S2;
            when S2 =>
                if dir = '0' then
                    s_data <= "00001111";
                else
                    s_data <= "11110000";
                end if;
                nState <= S3;
            when S3 =>
                if dir = '0' then
                    s_data <= "00111111";
                else
                    s_data <= "11111100";
                end if;
                nState <= S4;
            when S4 =>
                if dir = '0' then
                    s_data <= "11111100";
                else
                    s_data <= "00111111";
                end if;
                nState <= S1;
            when others => -- "Catch all" condition
                nState <= CLEAR;
                s_data <= (others => '0');
            end case;
        end case;
    end process;

    outData <= s_data;
end Behavioral;

```



# Final Remarks

---

At the end of this lecture you should be able to:

- Use a single clock signal for all the project's components
- Ensure proper system initialization (reset)
- Prefer synchronous over asynchronous reset
- Debounce inputs if required
- Describe FSMs in VHDL
- Decompose complex systems in datapath and controlpath

## To do:

- Test the given project on Nexys-4 kit
- Do lab. 4 part 1